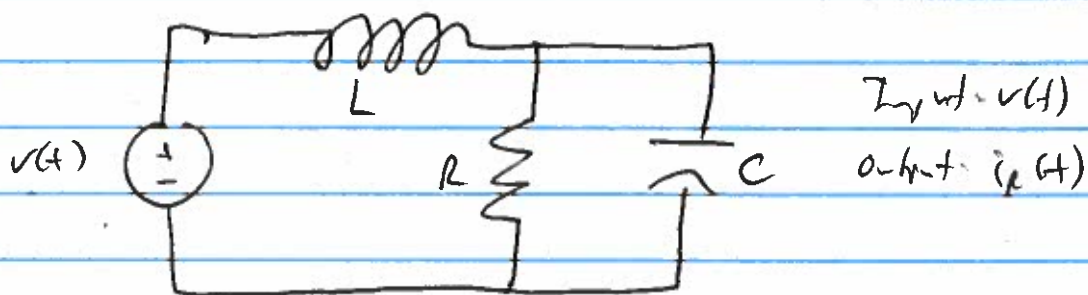


## State Space Representation of Electrical Network



$$V_L(t) = L \frac{di_L(t)}{dt} \Rightarrow \frac{di_L(t)}{dt} = \frac{1}{L} V_L(t)$$

$$V_C(t) = \frac{1}{C} \int_0^+ i_C(u) du$$

$$\frac{dV_C(t)}{dt} = \frac{1}{C} i_C(t)$$

State variables:  $V_C(t)$ ,  $i_L(t)$

Input variable:  $v(t)$

output variable:  $i_p(t)$

→ want to write  $di_L(t)/dt$  and  $dV_C(t)/dt$  in terms of state variables.

$$\frac{di_L(t)}{dt} = \frac{1}{L} V_L(t) = \frac{1}{L} v(t) - \frac{1}{L} V_C(t) \quad \checkmark$$

$$i_L(t) = i_R(t) + i_C(t)$$

$$i_R(t) = \frac{V_C(t)}{R} \Rightarrow i_C(t) = i_L(t) - \frac{V_C(t)}{R}$$

$$\frac{dV_c(t)}{dt} = \frac{1}{C} \left( i_L(t) - \frac{V_c(t)}{R} \right)$$

$$\text{So, } x(t) = \begin{bmatrix} V_c(t) \\ i_L(t) \end{bmatrix}$$

$$A = \begin{bmatrix} -\frac{1}{RC} & \frac{1}{L} \\ -\frac{1}{L} & 0 \end{bmatrix} \quad B = \begin{bmatrix} 0 \\ 1/L \end{bmatrix}$$

$$C = \begin{bmatrix} 1/R & 0 \end{bmatrix} \quad D = 0$$